


1. A 60-V source is connected across a 30-k  $\Omega$  resistance. (a) Draw the schematic diagram. (b) How much current flows through the resistance? (c) How much current flows through the voltage source? (d) If the resistance is doubled, how much is the current in the circuit?
2. A 12-V battery is connected across a 2-  $\Omega$  resistance. (a) Draw the schematic diagram. (b) Calculate the power dissipated in the resistance. (c) How much power is supplied by the battery? (d) If the resistance is doubled, how much is the power?
3. A picture-tube heater has 800 mA of current with 6.3 V applied. (a) Draw the schematic diagram, showing the heater as a resistance. (b) How much is the ~~R~~ resistance of the heater?
4. Convert the following units, using powers of 10 where necessary: (a) 12 mA to amperes; (b) 5000 V to kilovolts; (c)  $\frac{1}{2}$  M $\Omega$  to ohms; (d) 100,000  $\Omega$  to megohms; (e)  $\frac{1}{2}$  A to milliamperes; (f) 9000 microS to siemens; (g) 1000 microamps to milliamperes; (h) 5 k $\Omega$  to ohms; (i) 8 nanoseconds (ns) to seconds.
5. A current of 2 A flows through a 6- resistance connected across a battery. (a) How much is the applied voltage of the battery? (b) Calculate the power dissipated in the resistance. (c) How much power is supplied by the battery?
6. (a) How much resistance allows 30 A current with 6 V applied? (b) How much resistance allows 1 mA current with 10 kV applied? Why is it possible to have less current in (b) with the higher applied voltage?
7. A source of applied voltage produces 1 mA through a 10-M  $\Omega$  resistance. How much is the applied voltage?
8. Calculate the current  $I$ , in ampere units, for the following examples: (a) 45 V applied across 68 k $\Omega$  (b) 250 V across 12 M $\Omega$  (c) 1200 W dissipated in 600  $\Omega$ .
9. Calculate the  $IR$  voltage for the following examples: (a) 68 microA through 22 M $\Omega$ ; (b) 2.3 mA through 47 k $\Omega$ ; (c) 237 A through 0.012  $\Omega$ .
10. Calculate the resistance  $R$ , in ohms, for the following examples: (a) 134 mA produced by 220 V; (b) 800 W dissipated with 120 V applied; (c) a conductance of 9000 microS.

$$P = UI$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

$$P = UI$$

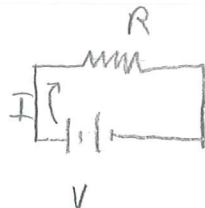

$$\left( \frac{V}{IR} \right)$$

$$V = I \cdot R$$

voltage = current  $\cdot$  resistance

volts = amps  $\cdot$  ohms

Brandon Buchanan  
Clifton

1. b  $I = \frac{V}{R}$   $I = \frac{60}{30000}$   $I = 0.002 \text{ a}$   $2 \text{ ma}$

c  $2 \text{ ma}$

d  $1 \text{ ma}$

2. b  $P = \frac{V^2}{R}$   $P = \frac{12^2}{2}$   $P = \frac{144}{2}$   $P = 72 \text{ w}$

c  $P = 72 \text{ w}$

d  $P = 36 \text{ w}$

3. b  $R = \frac{V}{I}$   $R = \frac{6300}{800}$   $R = 7.875 \Omega$

4. a  $0.012 \text{ a}$

b  $5 \text{ KV}$

c  $500,000$

d  $0.1 \text{ megohms } \Omega$

e  $500 \text{ ma}$

f  $0.009 \text{ s}$

g  $1 \text{ ma}$

h  $5,000,000 \Omega$

i  $0.0000000008 \text{ s}$

5. a  $12 \text{ V}$

b  $P = \frac{V^2}{R}$   $P = \frac{144}{6}$   $P = 24 \text{ w}$

c  $P = 24 \text{ w}$

6. a  $R = \frac{V}{I}$   $R = \frac{6}{30}$   $R = \frac{1}{5} \Omega$

b  $10,000,000 \Omega$

7.  $V = IR$   $V = 0.001(10,000,000)$   $V = 10,000 \text{ V}$

8. a  $I = \frac{V}{R}$   $I = \frac{75}{67000}$   $I = 16.62 \cdot 10^{-9} \text{ a}$

b  $I = \frac{V}{R}$   $I = \frac{250}{12000000}$   $I = 2.083 \cdot 10^{-5} \text{ a}$

c  $P = I^2 R$   $I = \pm \sqrt{\frac{P}{R}}$   $I = \pm \sqrt{\frac{1200 \text{ w}}{600 \Omega}}$   $I = \pm \sqrt{2} \text{ a}$

$I = 1.414 \text{ a}$

tera  
giga  
mega  
kilo  
milli  
micro  
nano  
pico

$$V = IR$$

$$P = VI$$

9.

a  $V = IR$   $V = 0.000068(220000000) \frac{0.02}{0.000068} V = 1996 V$

b  $V = IR$   $V = 0.0023(47000) V = 108.1 V$

c  $V = IR$   $V = 237(0.012) V = 2.844 V$

10.

a  $R = \frac{V}{I}$   $R = \frac{220}{0.139} R = 1691.79 \Omega$

b  $I = \frac{P}{V}$   $I = \frac{800}{120} I = 6.6 \Omega$

c  $\frac{1}{4000} \Omega$


$$V = IR$$

Ohm's Law  
SHOW ALL WORK


ComTech

Name Brandon Buchanan


1. Find the current.

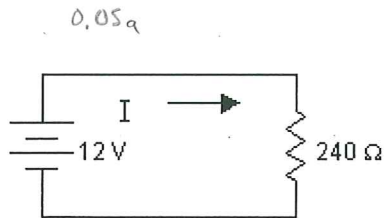


2. Find the Resistance

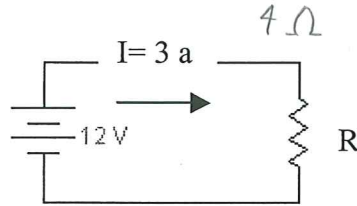

3. Find the voltage applied.

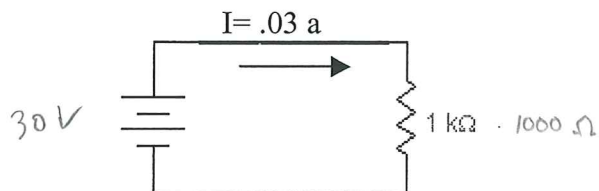

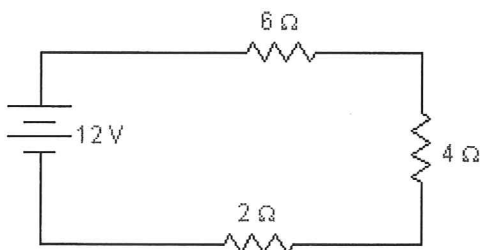4. Find the total resistance, the current in the circuit and the voltage drop across each resistor.



$$R_T = \underline{12 \Omega}$$


$$I_T = \underline{1 \text{ a}}$$

$$V_6 = \underline{6 \text{ V}}$$

$$V_4 = \underline{4 \text{ V}}$$

$$V_2 = \underline{2 \text{ V}}$$

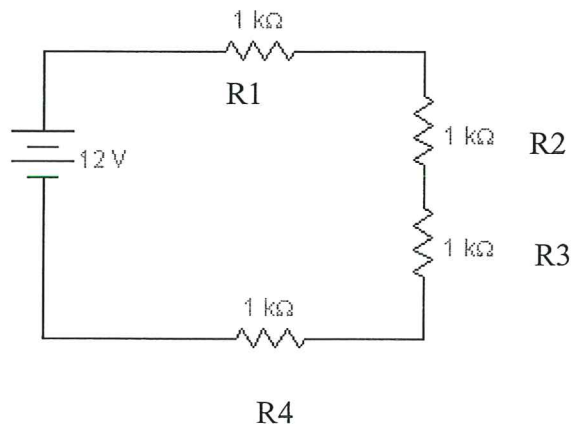5. Find the total resistance, the current in the circuit and the voltage drop across each resistor.



$$R_T = \underline{4000 \Omega}$$

$$I_T = \underline{0.003 \text{ a}}$$

$$V_1 = \underline{3 \text{ V}}$$

$$V_2 = \underline{3 \text{ V}}$$

$$V_3 = \underline{3 \text{ V}}$$

$$V_4 = \underline{3 \text{ V}}$$

Brandon Buchanan  
8.13.04

1.  $I_1 = \frac{V_T}{R_1}$   $I_1 = \frac{25}{500}$   $I_1 = 0.05 \text{ a}$   $I_2 = 0.05 \text{ a}$   
 $I_T = 0.1 \text{ a}$

2.  $I_1 = 1.33 \text{ a}$   $I_2 = 0.66 \text{ a}$   $I_3 = 0.33 \text{ a}$   $I_T = 2.33 \text{ a}$

3.  $V_T = 2000 \text{ V}$   $I_T = 8 \text{ a}$

4.  $V_T = 120 \text{ V}$   $I_2 = 2 \text{ a}$   $I_3 = 1 \text{ a}$   $I_T = 7 \text{ a}$

5.  $V_T = 1000 \text{ V}$   $R_2 = 250 \Omega$

6.  $V_T = 80 \text{ V}$   $R_3 = 18.46 \Omega$




$$V = IR$$


$$P = VI$$

\* series circuit - 1 Path and only one path for current

- current is same everywhere

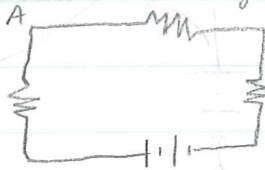

\* parallel circuits -

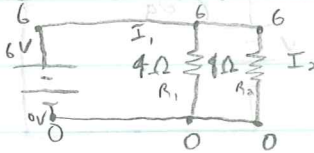

$$I_T = I_1 + I_2$$

$$I_T = \frac{V_T}{R_T} = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_T = 2\frac{2}{3} \Omega$$

$$\frac{1}{R_T} = \frac{1}{4\Omega} + \frac{1}{8\Omega}$$

$$\frac{1}{R_T} = \frac{2}{8} + \frac{1}{8}$$

$$I_T = \frac{V_T}{R_T}$$

$$I_T = \frac{6V}{\frac{8}{3}\Omega} = \frac{18V}{8\Omega}$$

$$I_T = 2.25 \text{ a}$$


$$I_1 = \frac{V_1}{R_1}$$

$$I_1 = \frac{6V}{4\Omega}$$

$$I_1 = 1.5 \text{ a}$$

$$I_2 = I_T - I_1$$

$$I_2 = 0.75 \text{ a}$$

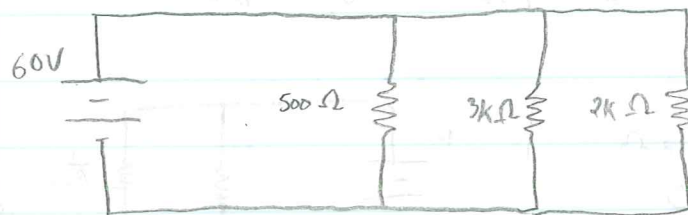

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{1}{500} + \frac{1}{3000} + \frac{1}{2000}$$

$$\frac{1}{R_T} = \frac{12}{6000} + \frac{2}{6000} + \frac{3}{6000}$$

$$\frac{1}{R_T} = \frac{17}{6000}$$

$$R_T = \frac{6000}{17}$$

$$R_T = 352 \Omega$$

$$I_T = \frac{V_T}{R_T}$$

$$I_T = \frac{60V}{352\Omega}$$

$$I_T = 0.17 \text{ a}$$

$$I_1 = \frac{V_1}{R_1}$$

$$I_1 = \frac{60V}{500\Omega}$$

$$I_1 = 0.12 \text{ a}$$

$$I_2 = \frac{V_2}{R_2}$$

$$I_2 = \frac{60V}{3000\Omega}$$




$$I_2 = 0.02 \text{ a}$$

$$I_3 = \frac{V_3}{R_3}$$

$$I_3 = \frac{60V}{2000\Omega}$$

$$I_3 = 0.03 \text{ a}$$

\* combination circuit -  
parallel

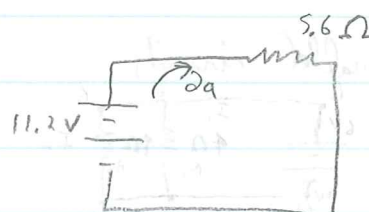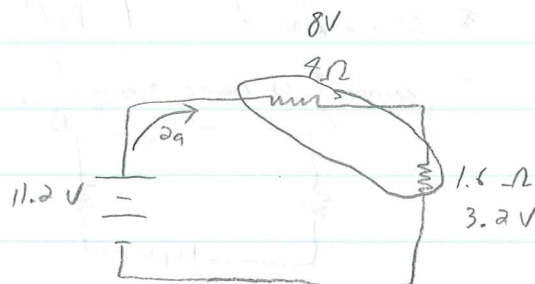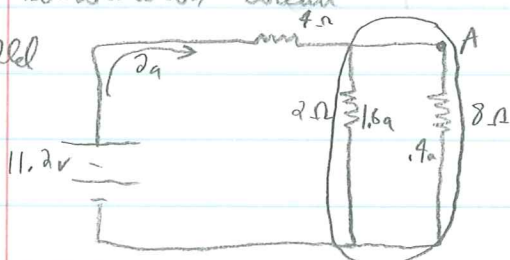

$$\frac{1}{R_{2,3}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{2,3}} = \frac{1}{2\Omega} + \frac{1}{8\Omega}$$

$$\frac{1}{R_{2,3}} = \frac{5}{8\Omega}$$

$$R_{2,3} = 1.6\Omega$$

$$\frac{1}{R_{1,2,3}} = \frac{1}{R_1} + \frac{1}{R_{2,3}}$$

$$\frac{1}{R_{1,2,3}} = \frac{1}{4\Omega} + \frac{1}{1.6\Omega}$$



$$\frac{1}{R_T} = \frac{1}{5.6\Omega}$$


$$I_T = \frac{V_T}{R_T}$$

$$I_T = \frac{11.2V}{5.6\Omega} \quad I_T = 2a$$


$$V_1 = \frac{I_1}{R_1} \quad V_1 = 2a \cdot 4\Omega \quad V_1 = 8V$$

$$I_2 = \frac{V_2}{R_2}$$

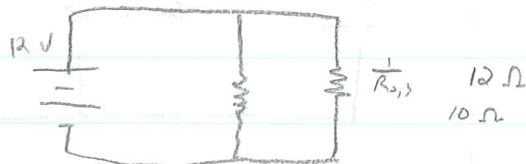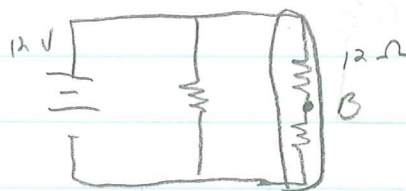


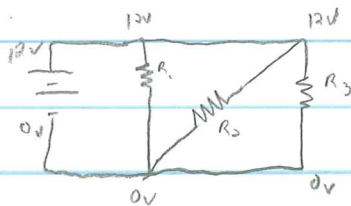

parallel circuit

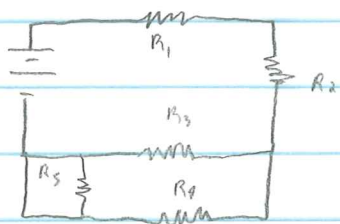

$R_1 + R_2 = \text{series}$

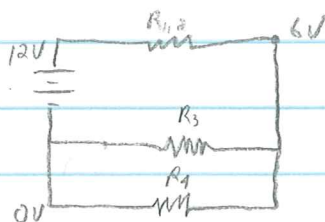

$R_5 = \text{dont need it}$



voltage is same


ITI

## Parallel Circuits


SHOW ALL WORK

Name *Brandon Paulanan*


1. Find  $I_T$ ,  $I_1$ , &  $I_2$

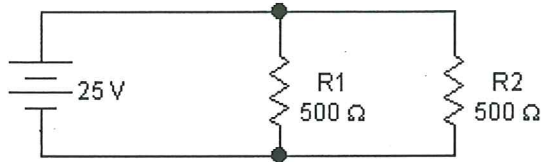

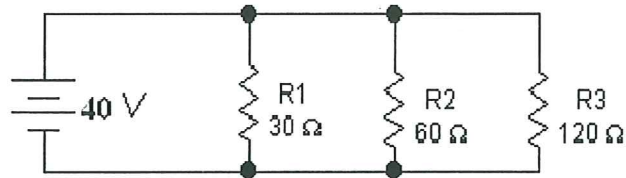
2. Find  $I_T$ ,  $I_1$ ,  $I_2$ , &  $I_3$



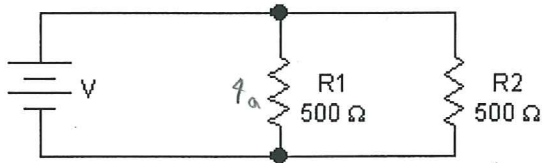
3. If  $I_1 = 4a$ , Find  $V$  and  $I_T$



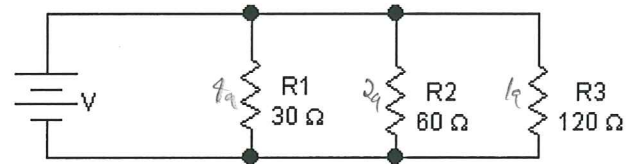
4. If  $I_1 = 4a$ , Find  $V$ ,  $I_T$ ,  $I_2$ , &  $I_3$



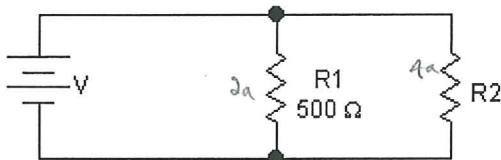5. If  $I_T = 6a$  and  $I_1 = 2a$ , find  $V$  &  $R_2$



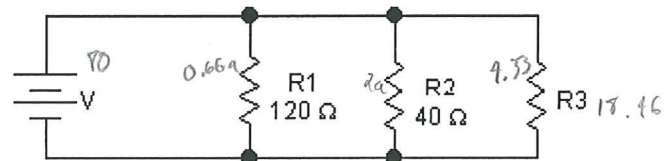6. If  $I_T = 7a$  and  $I_2 = 2a$ , find  $V$  &  $R_3$








# ComTech 2 Series & parallel Circuits

Name *Brandon Buchanan*

$$R_T = 18 \Omega$$

$$I_T = \frac{2}{3} A$$

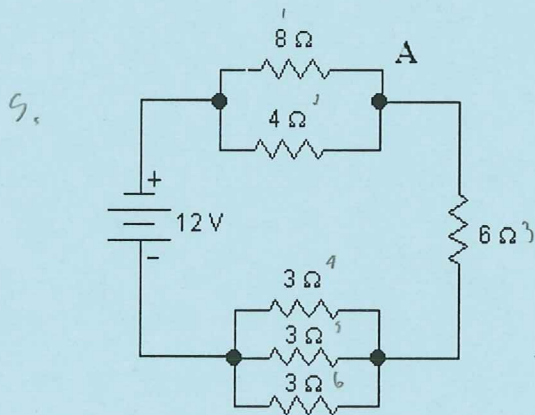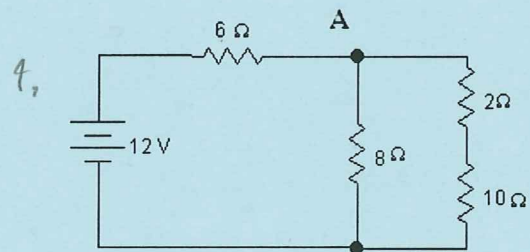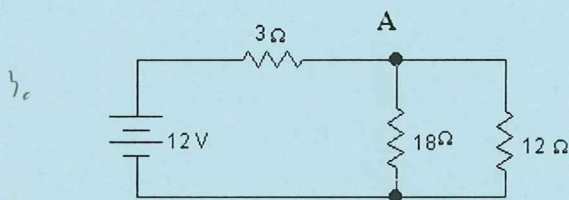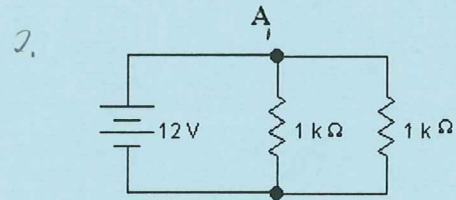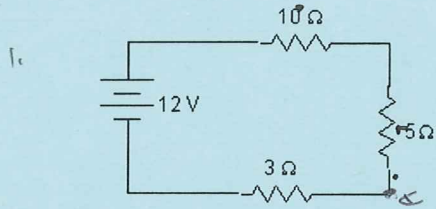

Find the **total resistance** and **total current** for each of the above circuits and the **voltage** at point A.

Steganos

PHLAK

Cain + Abel

Brandon Buchanan

1.

$$R_T = 18 \Omega$$


$$I_T = \frac{2}{3} A$$

2.

$$R_T = 2000 \Omega$$

$$I_T = 0.024 A$$

3.

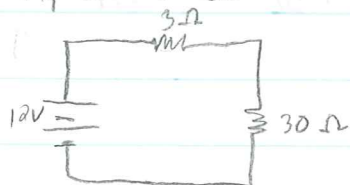


$$R_T = 33 \Omega$$

$$I_T = 0.36$$

$$V_A = 1.08 V$$

4.

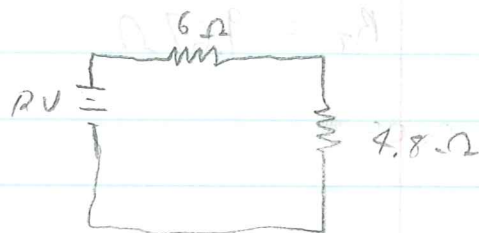

$$\frac{1}{R_T} = \frac{1}{8} + \frac{1}{12}$$

$$\frac{1}{R_T} = \frac{3}{24} + \frac{2}{24}$$

$$\frac{1}{R_T} = \frac{5}{24}$$

$$R_{2,3} = 4.8 \Omega$$

$$R_T = 10.8 \Omega$$

$$I_T = \frac{10}{9} A$$

$$V_A = \frac{10}{3} V = 3.3 V$$

$$5.9 V$$

5.



$$R_T = 9 \frac{2}{3} \Omega$$

$$I_T = 1.29 A$$

$$V_A = 8.7 V$$

5.

$$\frac{1}{R_{1,2}} = \frac{1}{9\Omega} + \frac{1}{8\Omega} \quad \frac{1}{R_{1,2}} = \frac{7}{3}\Omega$$

$$\frac{1}{R_{4,5,6}} = \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6} \quad \frac{1}{R_{4,5,6}} = \frac{1}{3\Omega} + \frac{1}{3\Omega} + \frac{1}{3\Omega}$$


$$\frac{1}{R_{4,5,6}} = \frac{3}{3\Omega} \quad R_{4,5,6} = 1\Omega$$

$$R_T = R_{1,2} + R_3 + R_{4,5,6}$$



$$R_T = 9.67\Omega$$

## Comp Arch


## Series & Parallel 2

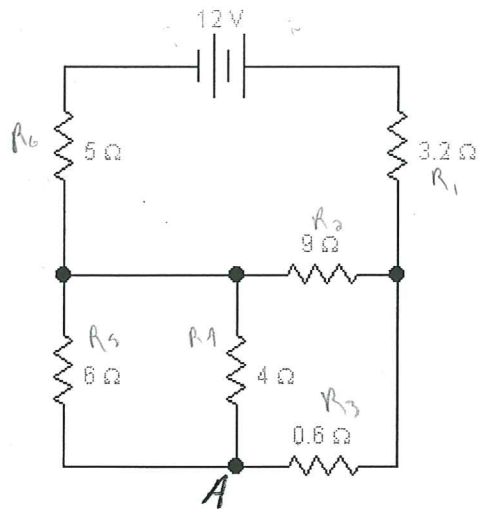

FIND  $R_T$  &  $V_A$

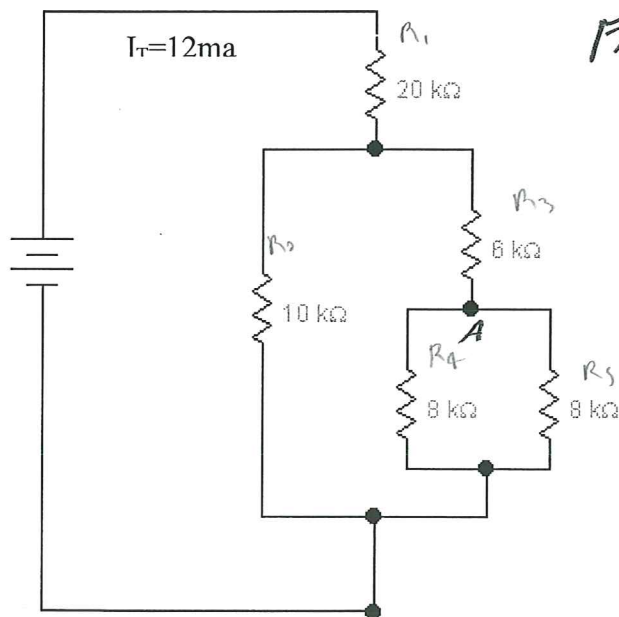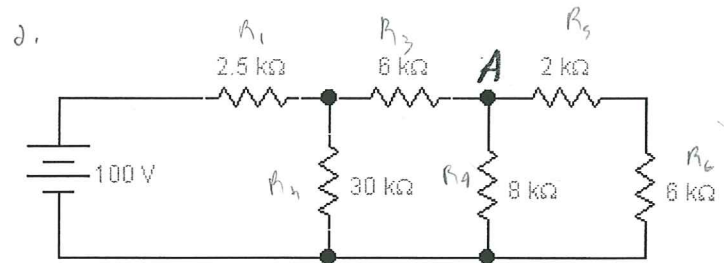

FIND  $V_T$  &  $V_A$

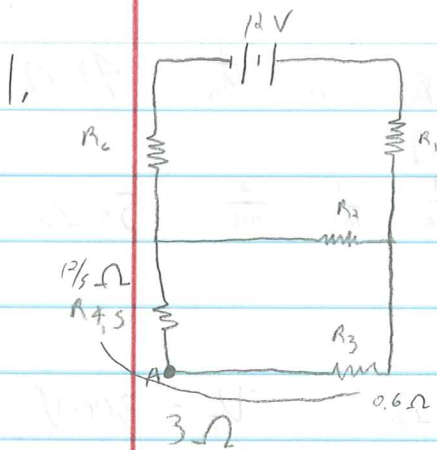

$$\frac{1}{R_{4,5}} = \frac{1}{6} + \frac{1}{4}$$

$$R_{4,5} = \frac{12}{5} \Omega$$

$$\frac{1}{R_{3,4,5}} = 0.6 \Omega + 2.4 \Omega$$


$$\frac{1}{R_{2,3,4,5}} = \frac{1}{9 \Omega} + \frac{1}{3 \Omega} = \frac{4}{9 \Omega}$$

$$\frac{1}{R_{7,5}} = \frac{2}{12} + \frac{3}{12}$$

$$\frac{1}{R_{9,5}} = \frac{5}{12} \Omega$$

$$\frac{1}{R_{3,4,5}} = 3 \Omega$$


$$\frac{9}{4} \Omega \quad 2.25 \Omega$$

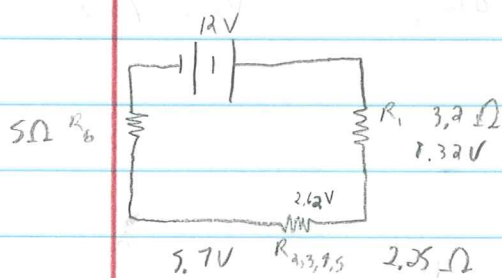

$$R_T = 10.45 \Omega$$


$$I_T = 1.15 \text{ A}$$
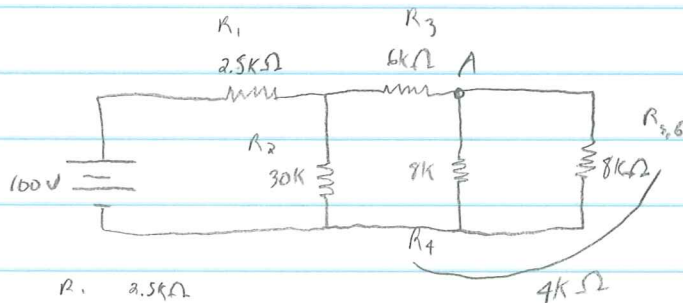
$$V_A = 5.7 \text{ V} \quad 7.8 \text{ V}$$



$$R_{4,5,6} = \frac{1}{8K} + \frac{1}{8K} = \frac{2}{8K} = 4K$$

$$R_{3,4,5,6} = 10K \Omega$$

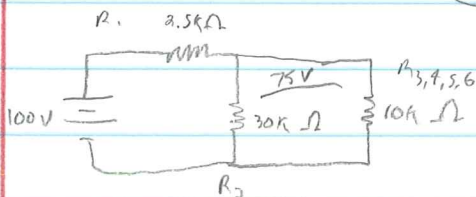

$$R_{2,3,4,5,6} = \frac{1}{30K} + \frac{1}{10K}$$

$$\frac{1}{30K} + \frac{3}{30K} = \frac{4}{30K} = \frac{30K}{4}$$

$$R_{2,3,4,5,6} = 7.5K \Omega$$

$$R_T = 10K \Omega$$


$$I_T = 0.01 \text{ A}$$

$$V_A = 20 \text{ V}$$






3.

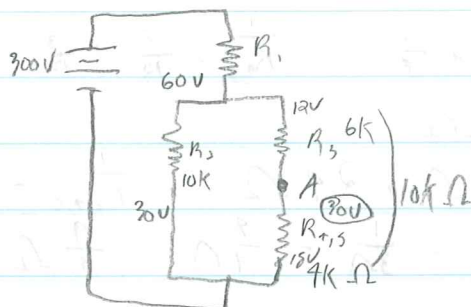

$$R_{4,5} = \frac{1}{8k} + \frac{1}{8k} = \frac{2}{8k} = \frac{1}{4k} = 4k \Omega$$

$$R_{2,4,5} = 10k \Omega$$
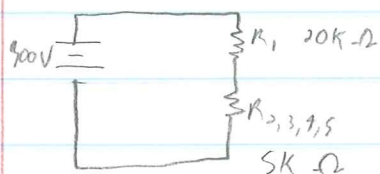
$$R_{2,3,4,5} = \frac{1}{10k} + \frac{1}{10k} = \frac{2}{10k} = 5k \Omega$$



$$R_T = 25000 \Omega$$

$$V_T = 300V$$

$$I_T = 0.012A$$


$$V_A = 98V$$

## \* \* Impedance

- opposes current changes
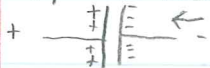
## \* Capacitors (measured in farads)

- opposes slow changes (allows faster changes) opposes DC




## \* Inductors (measured in Henrys)

- opposes fast changes (allows slow changes) opposes AC

- analog is AC


- stores energy in magnetic field

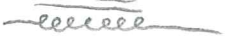-  iron core inductor

-  means variable

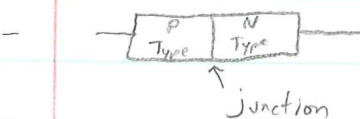
## \* Modifies Current Flow (semiconductors)

- diode - allows current to follow only one way way concept



- BJT - bipolar junction transistor

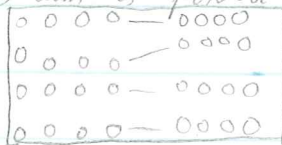
- Gallium is positive and Arsenic is negative




junction voltage is 70 V

0  
0  
0  
0

## \* BJT - Bipolar Junction Transistor

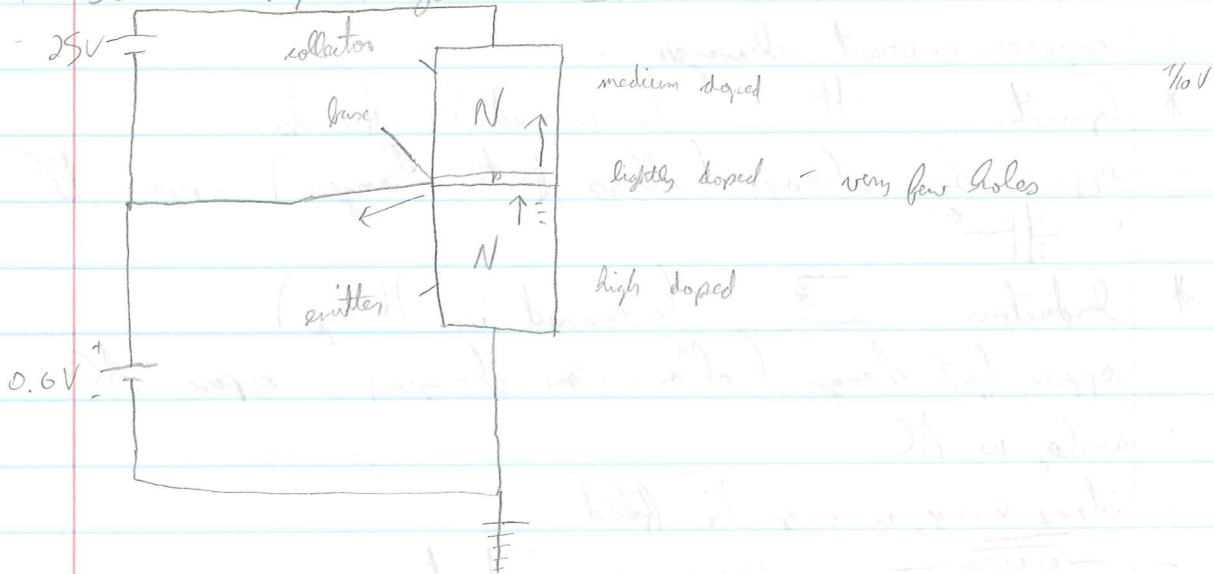

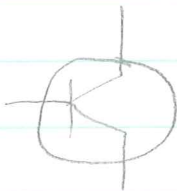- a transistor act as a voltage amplifier
- FET - field effect transistor
- MOS - metal oxide silicon (MOS - complementary...)
- anode is P side cathode is N side
- BJT



## - MOSFET - metal oxide silicon field effect transistor



\* a negative charge in gate pushes away

\*  $O^-$  flows in the gate

\* N Type

P Type

\* normally off & normally on

\* N Type depletion mode and enhanced mode


## Comp tech

(All work must be shown for credit) 6 pts ea.



$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{500} + \frac{1}{700} = \frac{12}{3500}$$

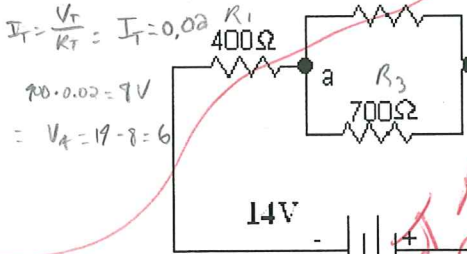
$$R_T = \frac{3500}{12} = 291\frac{2}{3} \Omega$$



$$R_1 \cdot I_T = V_1 \quad 400 \cdot 0.02 = 8V$$

$$V_R = V_T - V_1 = 14 - 8 = 6V$$

*You need to present this properly*

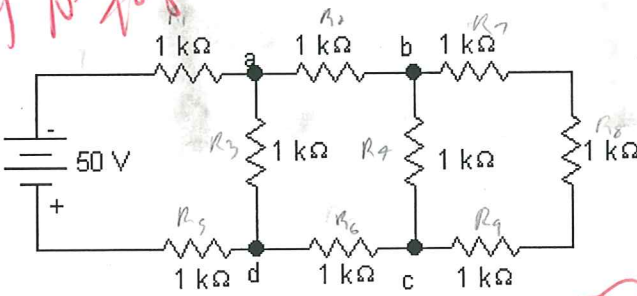

$$I_T = \frac{V_T}{R_T} = \frac{50}{2733\frac{1}{3}}$$

$$I_T = 0.018a$$

## Combo Circuits (Resistors)

1. For this figure, find:


The total resistance of the circuit  $691\frac{2}{3} \Omega$   
 The total current in the circuit  $0.02a$   
 The voltage at pt a  $6V$

2. For this figure, find:

The total resistance  $2733\frac{1}{3} \Omega$   
 The total Current  $0.018a$   
 The current in 1<sup>st</sup> vertical resistor (a-d)  $0.009$   
 The voltage at pt a  $32V$

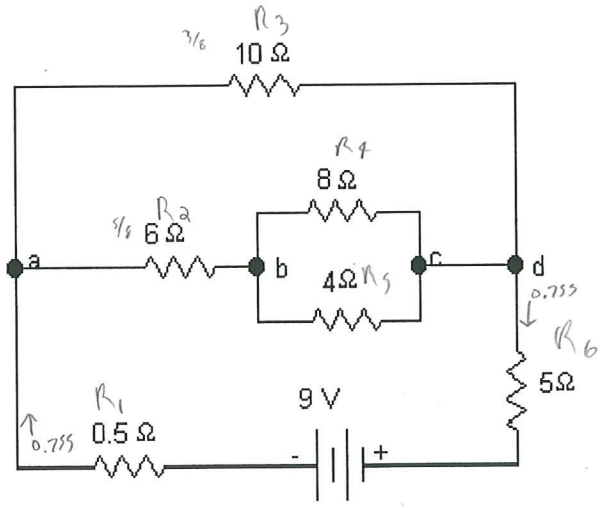3. For this figure, find:

The total resistance  $11.917 \Omega$   
 The total current  $0.755 \Omega$   
 The current in the  $4\Omega$   $0.189$   
 Voltage at pt d  $4.118V$



4. For below, find:

$$R_T = \frac{12 \Omega}{1a}$$

$$I_T = 1a$$


$$R_T = 6 + 4 = 10$$

$$R_T = 12$$

$$I_T = \frac{V_T}{R_T}$$

$$I_T = \frac{12}{12}$$


$$I_T = 1$$

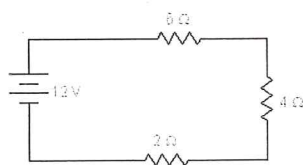

5. For below find:

$$R_T = \frac{17.143 \Omega}{2.333a}$$

$$I_T = 2.333a$$

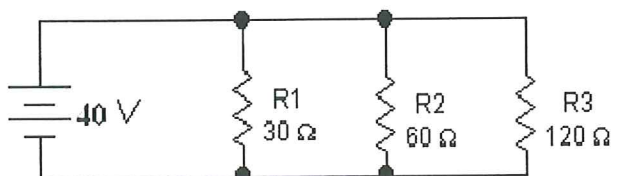


$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{30} + \frac{1}{60} + \frac{1}{120}$$

$$\frac{4}{120} + \frac{2}{120} + \frac{1}{120} = \frac{7}{120} = \frac{120}{7} = 17.143 \Omega$$

$$I_T = \frac{V_T}{R_T} = \frac{40}{17.143} = 2.333$$

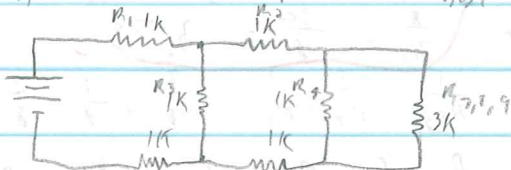
2.  $R_{7,8,9} = R_7 + R_8 + R_9$   $R_{7,8,9} = 1k + 1k + 1k = 3k$



$$\frac{1}{R_{7,8,9}} = \frac{1}{1000} + \frac{1}{3000} = \frac{4}{3000} = \frac{3000}{4} = 750 \Omega$$


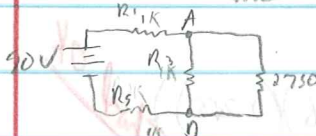
$$R_{2,4,6,7,8,9} = 1k + 1k + 750 = 2750 \Omega$$



$$\frac{1}{R_{2,4,6,7,8,9}} = \frac{1}{R_3} + \frac{1}{R_{2,4,6,7,8,9}} = \frac{1}{1000} + \frac{1}{2750} = \frac{11}{11000} + \frac{4}{11000} = \frac{15}{11000}$$


$$\frac{11000}{15} = 733 \frac{1}{3} \Omega$$



$$R_T = R_1 + R_5 + R_{2,4,6,7,8,9} = 1k + 1k + 733 \frac{1}{3} = 2733 \frac{1}{3}$$

\*  $V_D = V_T - (R_5(I_T))$   $V_D = 50V - (1k(0.18))$   $V_D = 50V - 18$   $V_D = 32$   
 $V_A = V_D - (R_3(I_T))$   $V_A = 32 - (733 \frac{1}{3}(0.018))$   $V_A = 32 - 13.19$   $V_A \approx 18V$

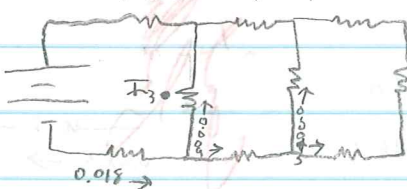$R_{2,4,6,7,8,9} = 733 \frac{1}{3}$  ... current should split





$$I_3 = 0.009$$

\*  $V_A' = V_T - V_A = V_A' = 50 - 18$

new voltage for  $V_A = 32V$



3.

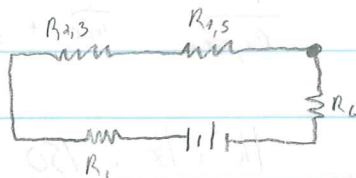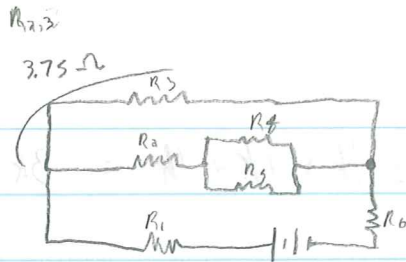

NOT 1/8

$$\frac{1}{R_{2,3}} = \frac{1}{R_2} + \frac{1}{R_3} \quad \frac{1}{R_{2,3}} = \frac{1}{6} + \frac{1}{10} = \frac{5}{30} + \frac{3}{30} = \frac{8}{30} = \frac{4}{15} \Rightarrow R_{2,3} = 3.75 \Omega$$

$$\frac{1}{R_{4,5}} = \frac{1}{R_4} + \frac{1}{R_5} = \frac{1}{8} + \frac{1}{4} = \frac{2}{8} + \frac{2}{8} = \frac{4}{8} = \frac{1}{2} \Rightarrow R_{4,5} = 2 \Omega$$

$$R_T = R_1 + R_{2,3} + R_{4,5} + R_6 = 0.5 + 3.75 + 2 + 5 = 11.25 \Omega$$


$$I_T = \frac{V_T}{R_T} = \frac{9}{11.25} = 0.8$$

$$V_D = V_T (V_1 + V_{2,3} + V_{4,5})$$

$$V_D = (0.8)(0.5) + (0.8)(3.75) + (0.8)(2) = 0.4 + 3.0 + 1.6 = 5.0$$

$$V_D = 0.4 + 3.0 + 1.6 = 5.0$$

$$V_D = 9 - (4.0) = 5.0$$

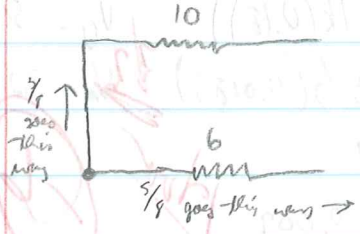

$$I_2 = I_T \left( \frac{5}{9} \right)$$


$$I_2 = 0.444$$

$$I_3 = I_T \left( \frac{3}{9} \right)$$

$$I_3 = 0.283$$

$$R_5 = I_2 \left( \frac{3}{2} \right)$$

$$R_5 = 0.189 \Omega$$

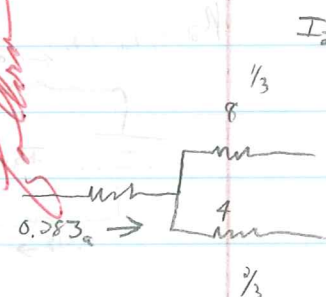

$$0.283 \rightarrow$$

1/3



## \* Charge

- positive - proton
- negative - electron
- measured in Coulombs
- $1 \text{ coulomb} = 6.25 \cdot 10^{18} \text{ electrons}$

## \* potential - measure of work

- available due to separation of charges
- $1 \text{ V} = \text{the work of } 1 \text{ joule separating a charge of } 1 \text{ coulomb}$

## \* current - flow of charges

- measured in amps
- $1 \text{ Amp} = \text{the flow of } 1 \text{ coulomb of charges past a point every second}$

- two types - electron current and conventional current

- electron current moves electrons; conductors

- conventional current moves holes; semiconductors

- holes = absence of electron

- resistance - opposition of current

- resistance is measured in Ohm's ( $\Omega$ )

- for electricity to be useful, it must have a complete path called a circuit

- functioning circuit is called closed circuit (complete path)

- open circuit has no path

- short circuit - when the path is circumvented

## \* Kinds of Electric Flow

- AC - alternate current, polarity changes

- DC - direct current, electron flows til end, constant polarity, batteries

- both types exist in a computer

- fans & motors run on AC

\* OHM's Law

-  $V = IR$

voltage = current  $\times$  resistance

- T, G, M, K

m,  $\mu$ , n, p

- milli, micro, nano, pico  
 $10^{-3}$   $10^{-6}$   $10^{-9}$   $10^{-12}$